

DDCO Assignment

Week 1

Basic Gates, Universal Gates, XOR, XNOR Gates
and Full Adder

Name : Renita Kurian

SRN : PES1UG20CS331

Roll No. : 27

Section : F

1. AND Gate

```
module and1(input wire A,B, output wire Y);  
  assign Y = A & B;  
endmodule
```

Testbench file –

```
module tb;  
  reg p,q;  
  wire z;  
  
  //instantiation  
  and1 a1(.A(p),.B(q),.Y(z));  
  initial begin  
    $dumpfile("and.vcd");  
    $dumpvars(0,tb);  
    end  
  
    initial begin  
      $monitor(p,q,z);  
      p=1'b0;  
      q=1'b0;  
      #5  
      p=1'b0;  
      q=1'b1;  
      #5  
      p=1'b1;  
      q=1'b0;  
      #5  
      p=1'b1;  
      q=1'b1;  
      #5  
      p=1'b0;  
      q=1'b0;  
      end  
endmodule
```

Output –


```
C:\PES1UG20CS331\iverilog\bin>iverilog -o and gates1.v TB_Gates.v

C:\PES1UG20CS331\iverilog\bin>vvp and
VCD info: dumpfile and.vcd opened for output.
000
010
100
111
000

C:\PES1UG20CS331\iverilog\bin>gtkwave and.vcd

GTKWave Analyzer v3.3.48 (w)1999-2013 BSI

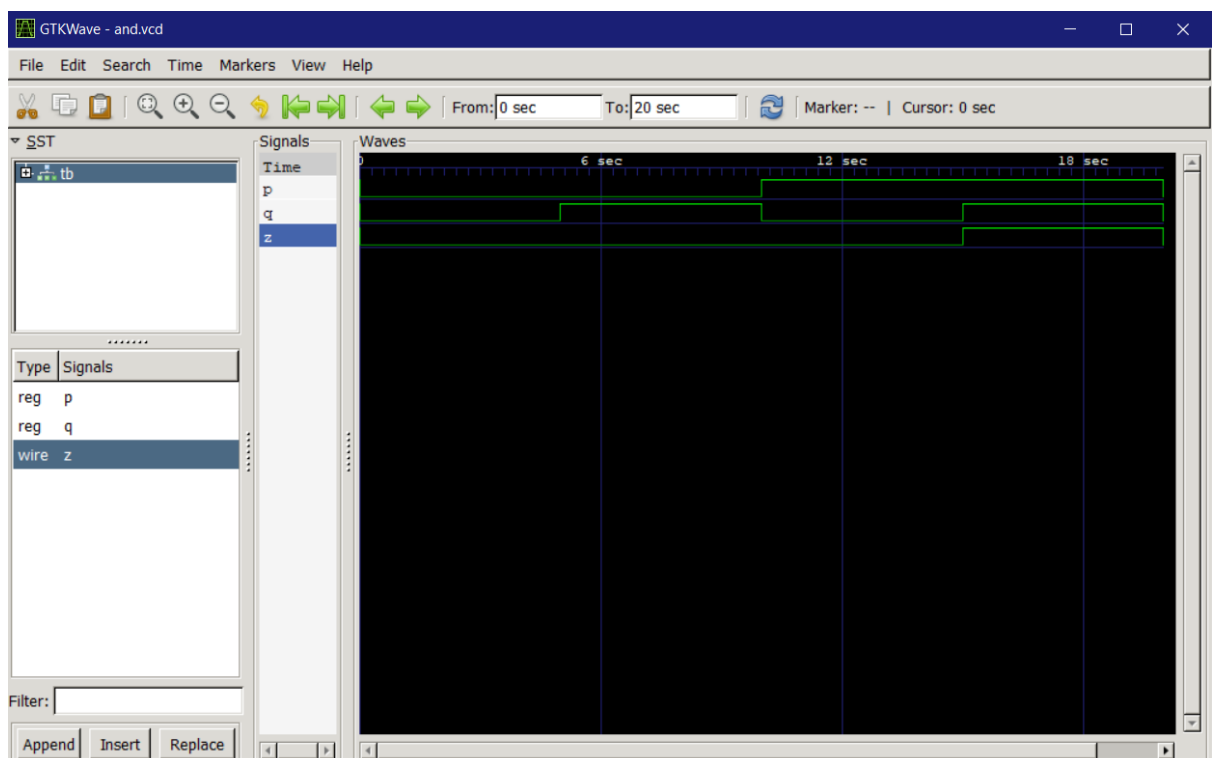[0] start time.
[20] end time.
WM Destroy
```



2. OR Gate


```
module or1(input wire A,B, output wire Y);  
  assign Y = A | B;  
endmodule
```

Testbench file —

```
module tb;  
  reg p,q;  
  wire z;  
  
  //instantiation  
  or1 a1(.A(p),.B(q),.Y(z));  
  initial begin  
    $dumpfile("or.vcd");  
    $dumpvars(0,tb);  
  end  
  
  initial begin  
    $monitor(p,q,z);  
    p=1'b0;  
    q=1'b0;  
    #5  
    p=1'b0;  
    q=1'b1;  
    #5  
    p=1'b1;  
    q=1'b0;  
    #5  
    p=1'b1;  
    q=1'b1;  
    #5  
    p=1'b0;  
    q=1'b0;  
  end  
endmodule
```

Output —
 
```
C:\PES1UG20CS331\iverilog\bin>iverilog -o or gates1.v TB_Gates.v  
  
C:\PES1UG20CS331\iverilog\bin>vvp or  
VCD info: dumpfile or.vcd opened for output.  
000  
011  
101  
111  
000
```



3. NOT Gate


```
module not1(input wire A, output wire Y);  
  assign Y=~A;  
endmodule
```

Testbench file –

```
module tb;  
  reg p;  
  wire z;  
  
  //instantiation  
  not1 a1(.A(p),.Y(z));  
  initial begin  
    $dumpfile("not.vcd");  
    $dumpvars(0,tb);  
  end  
  
  initial begin  
    $monitor(p,z);  
    p=1'b0;  
    #5  
    p=1'b1;  
    #5  
    p=1'b0;  
  end  
endmodule
```

Output –
 
```
C:\PES1UG20CS331\iverilog\bin>iverilog -o not gates1.v TB_Gates.v  
  
C:\PES1UG20CS331\iverilog\bin>vvp not  
VCD info: dumpfile not.vcd opened for output.  
01  
10  
01
```



4. NOR Gate


```
module nor1(input wire A,B, output wire Y);  
  wire x;  
  or1 a1(A,B,x);  
  not1 a2(x,Y);  
endmodule
```

Testbench file –

```
module tb;  
  reg p,q;  
  wire z;  
  
  //instantiation  
  nor1 a1(.A(p),.B(q),.Y(z));  
  initial begin  
    $dumpfile("nor.vcd");  
    $dumpvars(0,tb);  
  end  
  
  initial begin  
    $monitor(p,q,z);  
    p=1'b0;  
    q=1'b0;  
    #5  
    p=1'b0;  
    q=1'b1;  
    #5  
    p=1'b1;  
    q=1'b0;  
    #5  
    p=1'b1;  
    q=1'b1;  
    #5  
    p=1'b0;  
    q=1'b0;  
  end  
endmodule
```

Output –

```
C:\PES1UG20CS331\iverilog\bin>iverilog -o nor gates1.v TB_Gates.v  
  
C:\PES1UG20CS331\iverilog\bin>vvp nor  
VCD info: dumpfile nor.vcd opened for output.  
001  
010  
100  
110  
001
```

 5. NAND Gate


```
module nand1(input wire A,B, output wire Y);  
  wire x;  
  and1 a1(A,B,x);  
  not1 a2(x,Y);  
endmodule
```

Testbench file –

```
module tb;  
  reg p,q;  
  wire z;  
  
  //instantiation  
  nand1 a1(.A(p),.B(q),.Y(z));  
  initial begin  
    $dumpfile("nand1.vcd");  
    $dumpvars(0,tb);  
    end  
  
  initial begin  
    $monitor(p,q,z);  
    p=1'b0;  
    q=1'b0;  
    #5  
    p=1'b0;  
    q=1'b1;  
    #5  
    p=1'b1;  
    q=1'b0;  
    #5  
    p=1'b1;  
    q=1'b1;  
    #5  
    p=1'b0;  
    q=1'b0;  
    end  
endmodule
```

Output –
 
```
C:\PES1UG20CS331\iverilog\bin>iverilog -o nand gates1.v TB_Gates.v  
  
C:\PES1UG20CS331\iverilog\bin>vvp nand  
VCD info: dumpfile nand.vcd opened for output.  
001  
011  
101  
110  
001
```



6. XOR Gate

```
module xor1(input wire A,B, output wire C);  
  wire x,y,p,q;  
  not1 n1(A,x);  
  not1 n2(B,y);  
  and1 a1(B,x,p);  
  and1 a2(A,y,q);  
  or1 o1(p,q,C);  
endmodule
```

Testbench file –

```
module tb;  
  reg p,q;  
  wire z;  
  
  //instantiation  
  xor1 a1(.A(p),.B(q),.C(z));  
  initial begin  
    $dumpfile("xor.vcd");  
    $dumpvars(0,tb);  
  end  
  
  initial begin  
    $monitor(p,q,z);  
    p=1'b0;  
    q=1'b0;  
    #5  
    p=1'b0;  
    q=1'b1;  
    #5  
    p=1'b1;  
    q=1'b0;  
    #5  
    p=1'b1;  
    q=1'b1;  
    #5  
    p=1'b0;  
    q=1'b0;  
  end  
endmodule
```

Output –

```
C:\PES1UG20CS331\iverilog\bin>iverilog -o xor gates1.v TB_Gates.v
```

```
C:\PES1UG20CS331\iverilog\bin>vvp xor
VCD info: dumpfile xor.vcd opened for output.
000
011
101
110
000
```


```
C:\PES1UG20CS331\iverilog\bin>gtkwave xor.vcd
```

```
GTKWave Analyzer v3.3.48 (w)1999-2013 BSI
```

```
[0] start time.
```

```
[20] end time.
```

```
WM Destroy
```

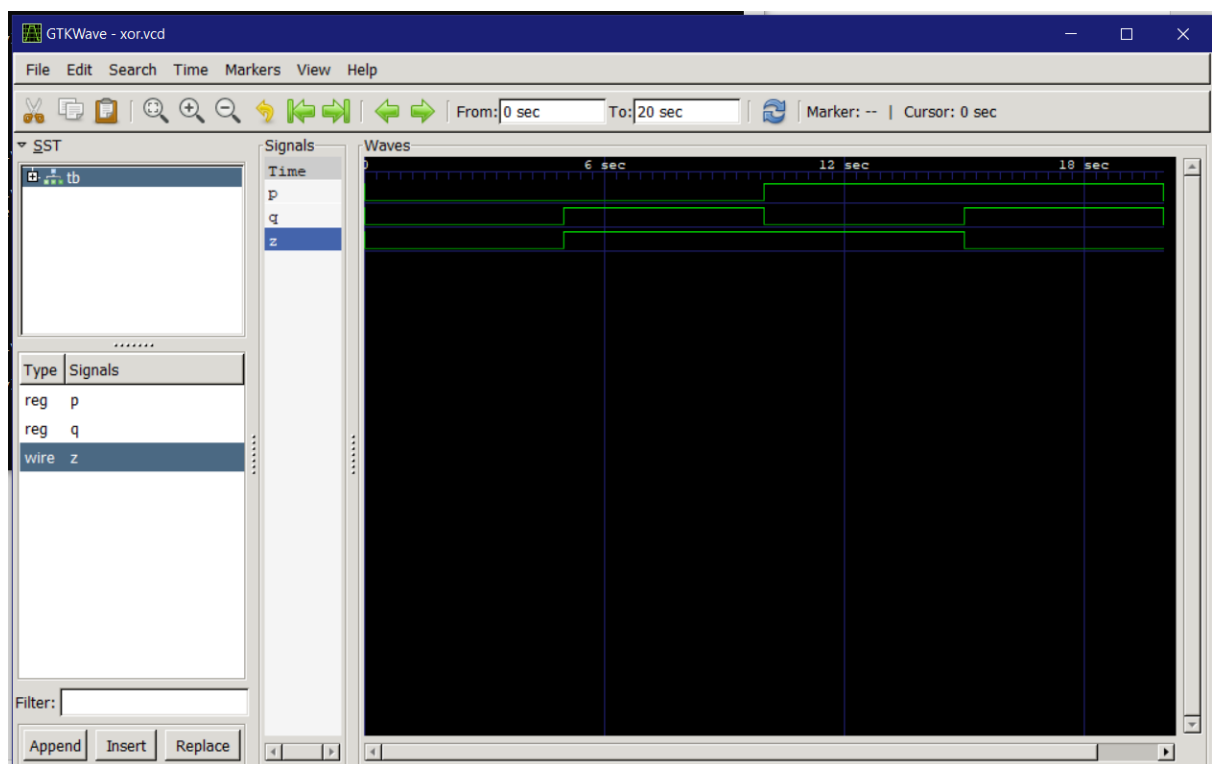

7. XNOR Gate

```
module xnor1(input wire A,B, output wire C);  
  wire x,y,p,q;  
  not1 n1(A,x);  
  not1 n2(B,y);  
  and1 a1(y,x,p);  
  and1 a2(A,B,q);  
  or1 o1(p,q,C);  
endmodule
```


Testbench file –

```
module tb;  
  reg p,q;  
  wire z;  
  
  //instantiation  
  xnor1 a1(.A(p),.B(q),.C(z));  
  initial begin  
    $dumpfile("xnor.vcd");  
    $dumpvars(0,tb);  
  end  
  
  initial begin  
    $monitor(p,q,z);  
    p=1'b0;  
    q=1'b0;  
    #5  
    p=1'b0;  
    q=1'b1;  
    #5  
    p=1'b1;  
    q=1'b0;  
    #5  
    p=1'b1;  
    q=1'b1;  
    #5  
    p=1'b0;  
    q=1'b0;  
  end  
endmodule
```

Output –

```
C:\PES1UG20CS331\iverilog\bin>iverilog -o xnor gates1.v TB_Gates.v

 C:\PES1UG20CS331\iverilog\bin>vvp xnor
VCD info: dumpfile xnor.vcd opened for output.
001
010
100
111
001
```



8. Full Adder

```
module fulladd(input wire a, b, cin, output wire sum, cout);
  wire [4:0] t;
  xor1 x0(a, b, t[0]);
  xor1 x1(t[0], cin, sum);

  and1 a0(a, b, t[1]);
  and1 a1(a, cin, t[2]);
  and1 a2(b, cin, t[3]);

  or1 o0(t[1], t[2], t[4]);
  or1 o1(t[3], t[4], cout);
endmodule
```

Testbench file —

```
module TB;
  reg aa,bb,cc;
  wire ss,cy;
  fulladd add1(.a(aa), .b(bb), .cin(cc), .sum(ss), .cout(cy));
  initial
  begin
    $dumpfile("dump.vcd");
    $dumpvars(0, TB);
    end

    initial begin $monitor(aa,bb,cc,ss,cy);
    aa = 1'b0;
    bb = 1'b0;
    cc=1'b0;
    #5
    aa = 1'b0;
    bb = 1'b1;
    cc=1'b1;
    #5
    aa = 1'b1;
    bb = 1'b0;
    cc=1'b0;
    #5
    aa = 1'b1;
    bb = 1'b1;
    cc=1'b0;
    #5
    aa = 1'b0;
    bb = 1'b0;
    cc=1'b1;
    #5
    aa = 1'b0;
    bb = 1'b0;
    cc=1'b0;
    end
endmodule
```


Output –

```
C:\PES1UG20CS331\iverilog\bin>iverilog -o fa gates1.v fulladd.v TB_FA.v

C:\PES1UG20CS331\iverilog\bin>vvp fa
VCD info: dumpfile dump.vcd opened for output.
00000
01101
10010
11001
00110
00000

C:\PES1UG20CS331\iverilog\bin>gtkwave dump.vcd

GTKWave Analyzer v3.3.48 (w)1999-2013 BSI

[0] start time.
[25] end time.
WM Destroy
```

